

YASH SARANG

DGAD / 47


DLCOA

EXPERIMENT / ASSIGNMENT - 2

Sarangadh

Teacher's Sign:

Assignment 2

 

A	B	C	D	A.B.C.D
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1


② A universal gate is a gate which can implement any Boolean function without need to use any other gate type. The NAND Gate & NOR Gate are universal gates. This is advantageous, since NAND & NOR gates are economical & easier to fabricate & are the basic gates using the in all IC digital logic families.

③ AND \rightarrow Boolean expression of AND gate $Y = A \cdot B$.

OR \rightarrow Boolean express is $Y = A + B$.

NAND \rightarrow Boolean expression is $Y = \overline{A \cdot B}$

NOR \rightarrow Boolean expression is $Y = \overline{A + B}$.

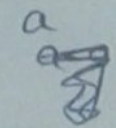④ De Morgan's theorem describes the equivalence between gates with inverted inputs & gates with inverted outputs. Simply put a NAND gate is equivalent to Negative-OR gate and NOR gate is equivalent to  Negative-AND gate.


⑤ NAND gate is considered as a universal gate, it can be designed of any digital circuitry.

The minimum number of NAND gates required to design a half adder is 5.

The first NAND gate takes the inputs which are the two 1-bit numbers. The resultant NAND operated inputs will be again given to as input to 3- NAND gates along with the original input.

Out of the 3 considered NAND gates, the third NAND gate will generate the carry bit.

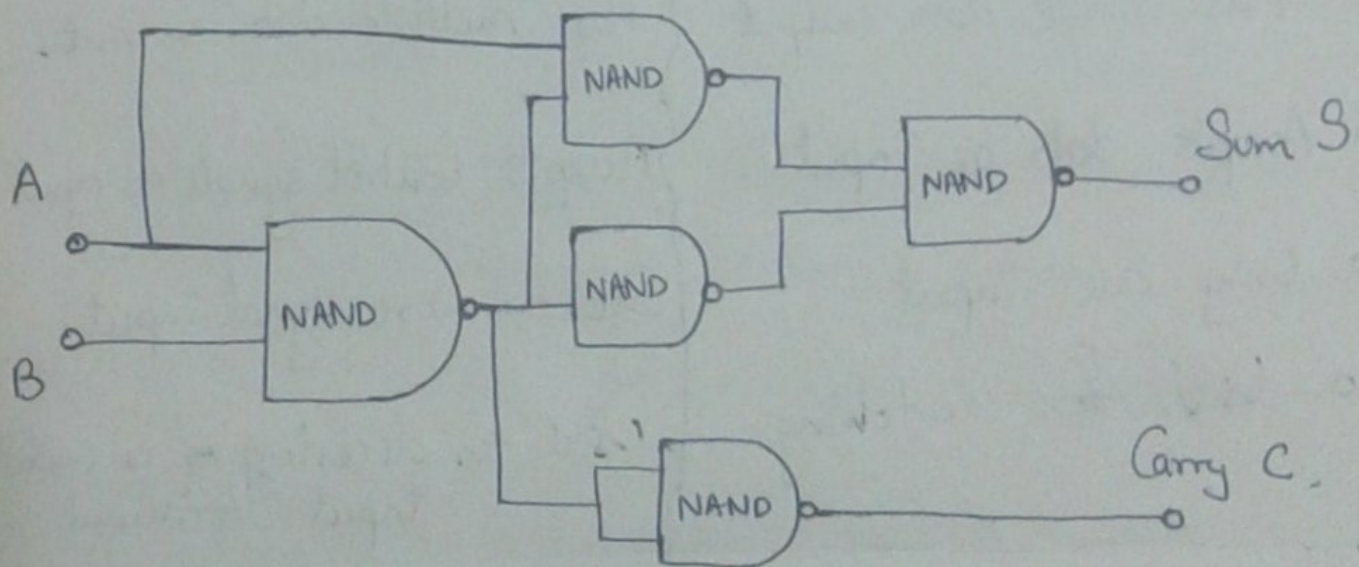The NAND operation can be understood more clearly with the given diagram.



⑥ Demultiplexer (DEMUX)

It is a combinational logic circuit designed to switch one common input line to one of several separate output line. The data distributor is commonly known as Demultiplexer.

Multiplexer

- Multiplexer process the digital info from various source into a single source.
- Known as data selector
- It is a digital switch.
- Has multiple data input
- Has single data output
- Accepts data as input
- Only one input
- Used for switching

Demultiplexer


- It receives digital info from a single source and converts into several sources
- Known as data distributor.
- It is a digital circuit-
- Has single data input.
- Has multiple data output.
- Accepts control signals as input
- One or more signal input.
- Used for decoding of encoded input terminal.

7) Define half subtractor & full subtractor.

(i) Half subtractor,

It is a combined circuit which is used to perform subtraction of two bits. It has two inputs, X (minuend) & Y (subtrahend) and two outputs D (difference) & B (borrow).

Diagram/Symbol:

 


Truth table:

X	Y	D	B
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

 (ii) Full subtractor


It is a combinational circuit that performs subtraction including 3 bits namely minuend, subtrahend, and borrowin. The logic symbol & truth table are shown.



Truth table:

X	Y	Bin	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 - ⑧ Full adder is added which add 3 inputs & produces 2 outputs. The two inputs are A & B, and input carry as C-IN output carry is designed as C-OUT & the normal output is designated as S which is SUM.




Logical Expression.


$$A'B'C-IN + A'BC-IN' + AB'C-IN' + ABC-IN$$

$$= C-IN(A'B' + AB) + C-IN'(A'B + AB')$$
 
$$= C-IN \text{ XOR } (A \text{ XOR } B)$$



Full adder logic circuit.

 

⑩ Algorithm:-

- Register, $M \leftarrow \text{Divisor}$
- Register, $Q \leftarrow \text{Dividend}$
- Register, $AC \leftarrow 0$
- Register, $C \leftarrow 0$ (1-bit carry)
- Count $\leftarrow n$ [size of register]

Initial values

Restoring:

1. Shift C, AC, Q , left by 1 bit.
- 2) $AC \leftarrow AC - M$ [subtraction & checking the sign can be used for comparison]
- 3) If the sign of AC is negative (i.e. $C=1$)
 set Q_0 & add M back to AC , otherwise
 set Q_0 to 1.

Non Restoring:

- 1) Do the following n times.
 If the sign of AC is positive ($C=0$) then shift
 C, AC & Q left one bit & subtract M from AC .
 else
 shift C, AC & Q left one bit position & add M
 to AC .
 If the sign of AC is positive then
 Set q_0 to 1
 else
 Set q_0 to 0
- 2) If the sign of AC is positive,
 then add M to AC .

Non Restoring Division Algorithm

N	M	A	Q	Action
4	00011	00000 00001 11110	1011 011_ 011_	Start Left shift AQ $A = A - M$
3	00011	11110 11100 11111	0110 110_ 110_	$Q[0] = 0$ Left shift AQ $A = A + M$
2	00011	11111 11111 00010	1100 100_ 100_	$Q[0] = 0$ Left shift AQ $A = A + M$
1	00011	00010 00001 00010	1001 001_ 001_	$Q[0] = 1$ Left shift AQ $A = A - M$
0	00011	00010	0011	$Q[0] = 1$

From calculations we get,

$$\text{Quotient (Q)} = 3$$

$$\text{Remainder (A)} = 2$$

Examples : Perform Division Restoring Algorithm.

Dividend = 11 , Divisor = 3.

Restoring Division Algorithm

n	M	A	Q	Operation
4	00011	00000	1011	initialize
	00011	00001	011_	shift left AQ
	00011	11110	011_	$A = A - M$
	00011	00001	0110	$Q[0] = 0$ & restore A
3	00011	00010	110_	shift left AQ
	00011	11111	110_	$A = A - M$
	00011	00010	1100	$Q[0] = 0$
2	00011	00101	100_	shift left AQ
	00011	00010	100_	$A = A - M$
	00011	00010	1001	$Q[0] = 1$
1	00011	00101	001_	shift left AQ
	00011	00010	001_	$A = A - M$
	00011	00010	0011	$Q[0] = 1$

Register Q contains the quotient i.e 3. and register A contains remainder 2.