

YASH SARANG

D6AD

47

DLCOA / Experiment 11

Aim: To design an arithmetic logic unit Software Used: DLCOA virtual lab simulator

Theory: In computing, an arithmetic logic unit (ALU) is a combinational digital circuit that performs arithmetic and bitwise operations on integer binary numbers. The inputs to an ALU are the data to be operated on, called operands, and a code indicating the operation to be performed; the ALU's output is the result of the performed operation. In many designs, the ALU also has status inputs or outputs, or both, which convey information about a previous operation or the current operation, respectively, between the ALU and external status registers.

Design issues: The circuit functionality of 1-bit is shown here, depending upon the control signal S1 and S0, the circuit operates as:

S1 = 0, S0 = 0 : Output = A.B

S1 = 0, S0 = 1 : Output = A+B

S1 = 1, S0 = 0 : Output = $\sim A.B + A.\sim B$

S1 = 1, S0 = 1 : Output = A add B


Objective: Objective of 4-bit Arithmetic logic unit (with AND, OR, EXOR, ADD Operation):

1) Understanding behaviour of ALU from working module and the module designed by the student as part of the experiment.


2) Designing an ALU to give parameter. Conclusion: We have studied ALU and thereafter designed it in the virtual simulator and verified it.

PROCEDURE:

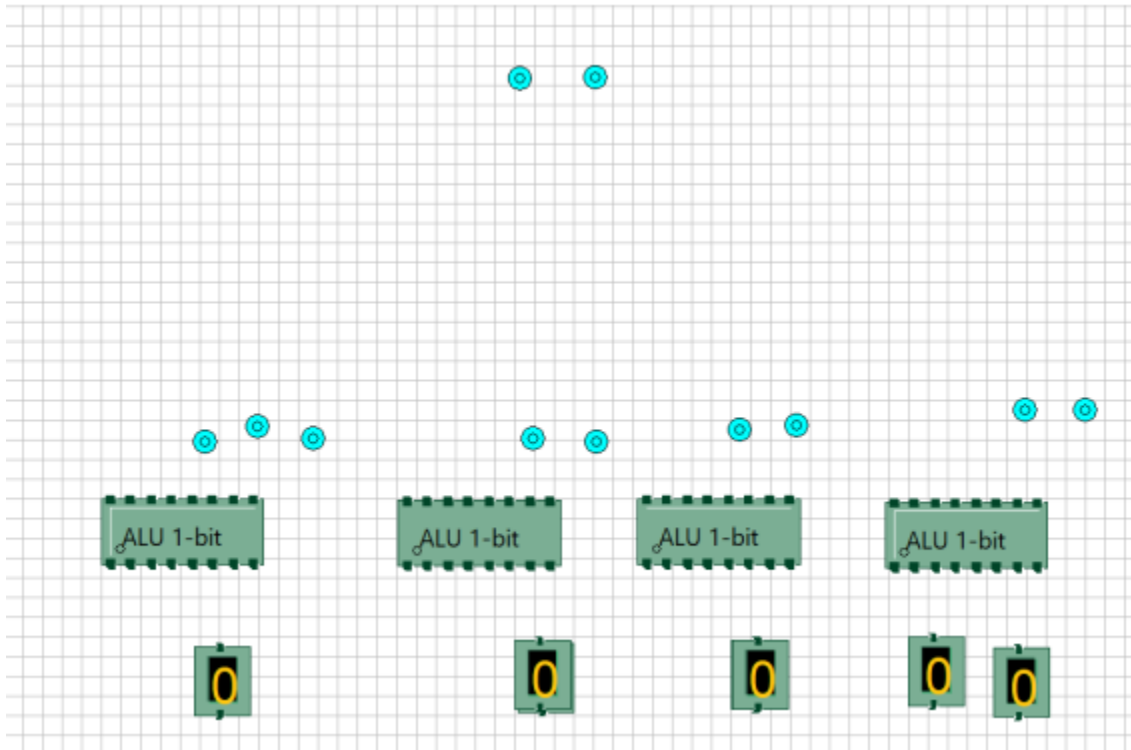1. Select four 1-bit ALU from the “Other Components” menu. 5-bit displays and 11 bit switches from Input/Output and arrange them as shown below.



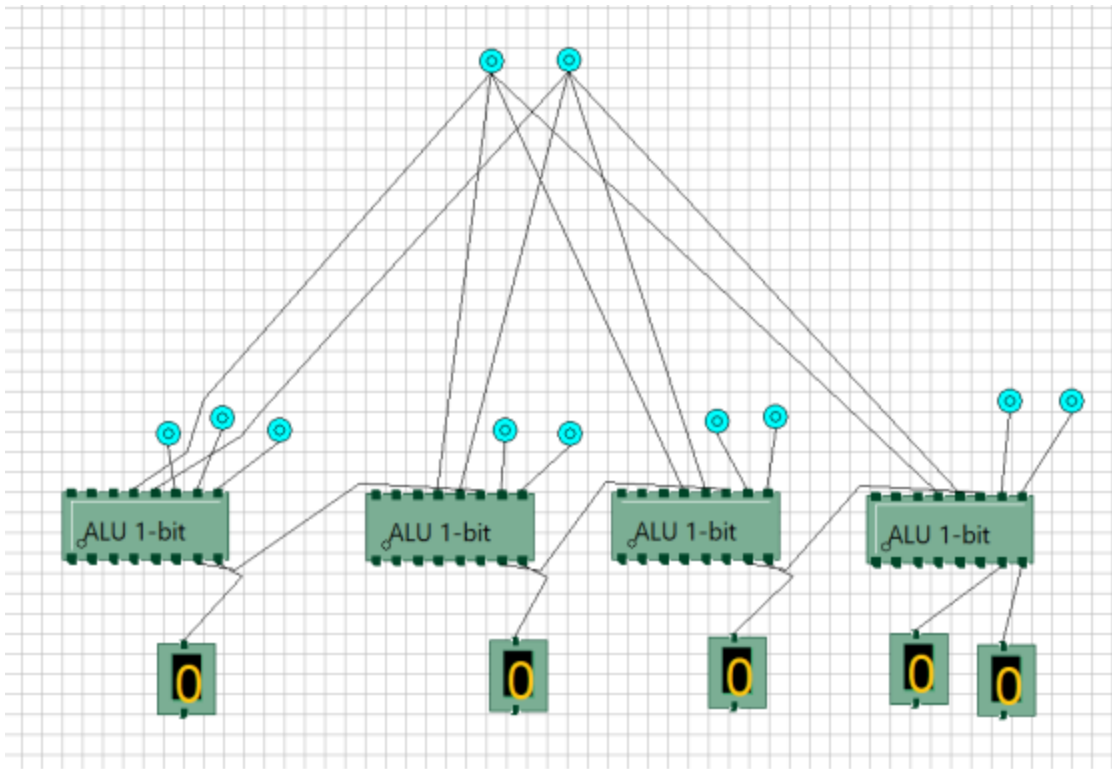2. Connect all the components using the Connection tool as shown below.



OUTPUT:

