

VASH SARANG

47 / DGAD

DLCOA

Experiment 8.

Experiment 8

Aim: Study of flip flops using IC's.

Apparatus:	Sr no.	Components
	1	JK Flip flop.
	2	D Flip flop
	3	SR Flip flop.

Theory: Flip flops are the basic single-bit memory elements used to build sequential circuits with one or two inputs/outputs, designed using individual logic gates & feedback loops.

JK Flip Flop.

Characteristic eqn of JK flip flop is:

$$Q_{\text{next}} = J\bar{Q} + \bar{K}Q$$

Preset (PRE) and clear (CLR) are as asynchronous active low inputs and operate immediately of the clock input.

D Flip Flop.

Characteristic eqn of D flip flop is $Q_{\text{next}} = D$.

Following the hold time ~~to~~ interval, data at the D inputs may be changed without affecting levels of output.

Truth Tables: JK Flip Flop.

Q _K	J	K	Q _{next}
0	x	x	Q _n
1	0	0	Q _n
1	0	1	0
1	1	0	1
1	1	1	$\overline{Q_n}$

SR Flip Flop	Q _K	S	R	Q _{next}	
	0	x	x	Q _n	Memory
	1	0	0	Q _n	Hold state
	1	0	1	0	Reset
	1	1	0	1	Set
	1	1	1	Invalid	Unused

D Flip Flop	Q _K	D	Q _{next}	
	0	x	Q _n	- Memory
	1	0	0	} Buffer.
	1	1	1	


T Flip Flops	Q _K	T	Q _{next}	
	0	x	Q _n	Memory
	1	0	Q _n	Hold
	1	1	$\overline{Q_n}$	Toggle.

SR Flip Flop.


The SR flip flop is a 1 bit memory device having two inputs i.e. SET & RESET.

The SR flip flop stands for 'Set-Reset' flip flop. The reset input is used to get back the flip flop to its original state from the current state with an output Q .

Block diagram:

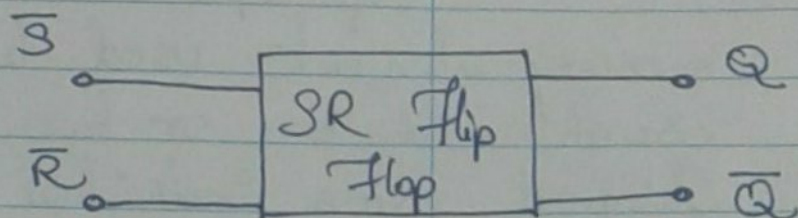

Circuit diagram.

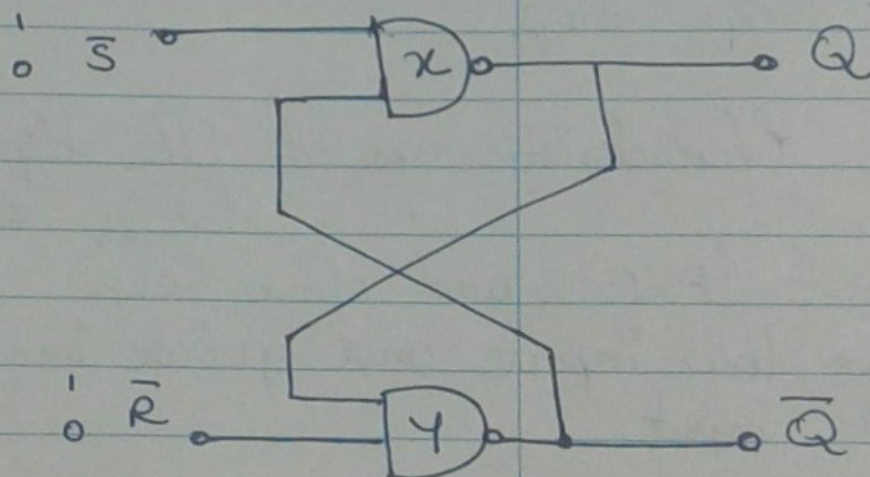


Toggle Flip Flop.


In T-Flip Flop, 'T' defines the term "Toggle". In SR Flip Flop, we provide only a single input called "Toggle" or "Trigger" to input to avoid an intermediate state occurrence.

Now, flip flop work as a Toggle switcher.

Block diagram:

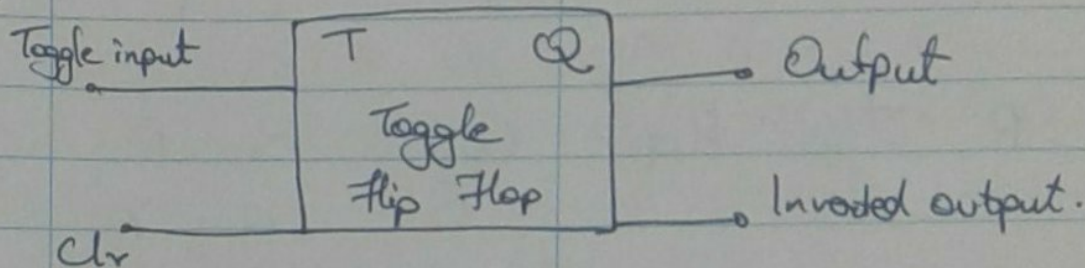

Circuit diagram:

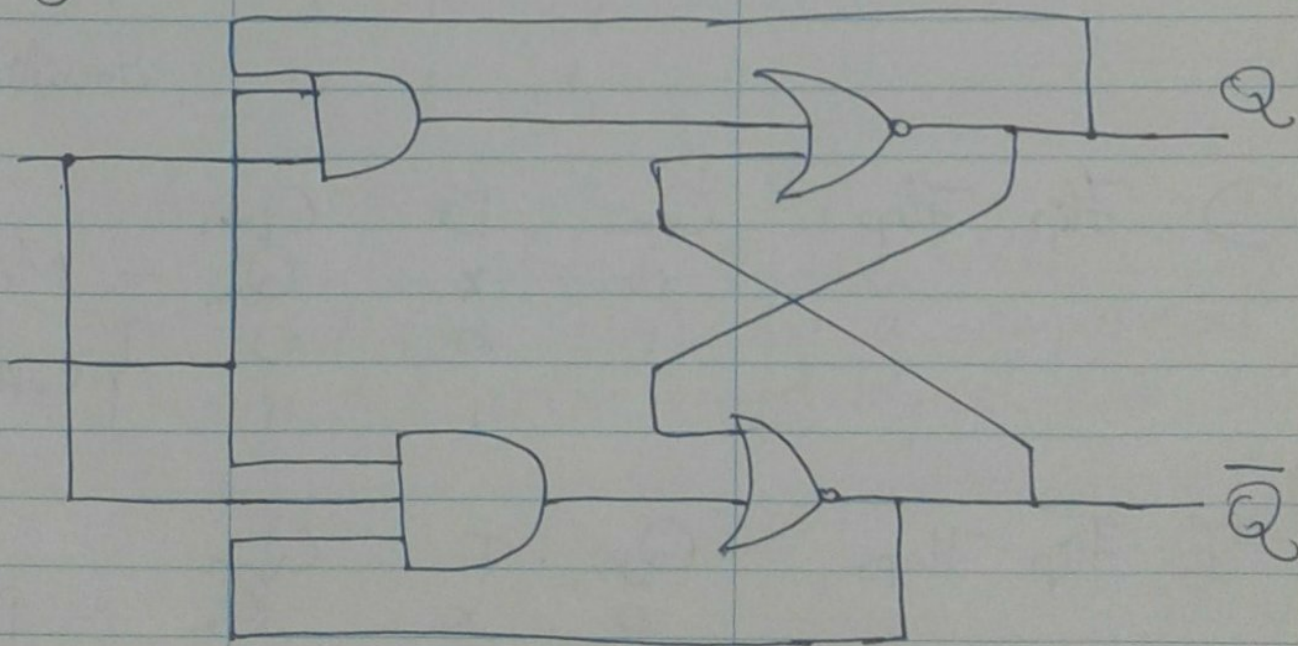

The T flip flop is toggled when the set & resets inputs alternatively changed by the incoming trigger.

Procedure:

- ① Mount the required IC's on the bread board and make the connections as per the diagram.
- ② Give the +5 vcc & Gnd to IC with the help of connecting wires.
- ③ With the connecting wires, give the logical inputs to the required pins.
- ④ Connect the outputs ~~pin~~ across the logical output terminals (Q , Q_{bar}).
- ⑤ Apply different inputs and verify the truth table.

Conclusion:

Various flip-flops were studied using IC's and their truth tables were verified.